

HA 179L10(P),A(PA)	Z-IC	-10V, 0,15A, $\pm 4\%$ , A= $\pm 2\%$	7a	-		
HA 179L12(P),A(PA)	Z-IC	-12V, 0,15A, $\pm 4\%$ , A= $\pm 2\%$	7a	79L12/T0-92	7a	
HA 179L15(P),A(PA)	Z-IC	-15V, 0,15A, $\pm 4\%$ , A= $\pm 2\%$	7a	-		
HA 179 L05...L15UA	Z-IC	=HA 179L05...L15: SMD	39a	-		
HA 179 M05 FM,FMP	Z-IC	Iso, -5V, 0,5A	17c	(7905/T0-220)	17c	3
HA 179 M06 FM,FMP	Z-IC	Iso, -6V, 0,5A	17c	-		
HA 179 M06 FM,FMP	Z-IC	Iso, -12V, 0,5A	17c	(7912/T0-220)	17c	3
HA 179 M15 FM,FMP	Z-IC	Iso, -15V, 0,5A	17c	(7915/T0-220)	17c	3
HA 1107	LIN-IC	VC, Ton-ZF	-	-		
HA 1108	LIN-IC	TV-AFT	14-DIP	-		
HA 1124	LIN-IC	TV, Ton-ZF, NF-Tr	14-DIP	-		
HA 1125	LIN-IC	TV, Ton-ZF, NF-Tr	14-DIP	-		
HA 1126	LIN-IC	TV-AFT	14-DIP	-		**
HA 1127(P)	LIN-IC	TV, 5x Trans.-Array, 20V, 50mA, 460MHz	14-DIP	-		
HA 1127 FP	LIN-IC	=HA 1127(P): SMD	14-MDIP	-		
HA 1137(W)	LIN-IC	FM-ZF, NF-V, AFC	16-DIP	-	16-DIP	**
HA 1138	LIN-IC	AM-V/M/O/ZF + Dem	16-DIP	-		**
HA 1144	LIN-IC	TV, Video-ZF	14-DIP	-		**
HA 1151	LIN-IC	AM-HF + ZF	14-DIP	-	14-DIP	**
HA 1156(W)	LIN-IC	Stereo-Decoder	14-DIP	-		**
HA 1166(W)	LIN-IC	-	-	-		**
HA 1167	LIN-IC	-	-	-		**
HA 1190	LIN-IC	Sensor f. 4 Tasten/keys	16-DIP	SAS 560 S	16-DIP	
HA 1194	LIN-IC	Sensor f. 4 Tasten/keys	16-DIP	SAS 570 S	16-DIP	
HA 1196	LIN-IC	Stereo-Decoder	16-DIP	-		**
HA 1197	LIN-IC	AM-Tuner + ZF	16-DIP	HA 1197	16-DIP	*
HA 1199	LIN-IC	AM-Tuner	16-DIP	HA 1199	16-DIP	*
HA 1201	LIN-IC	FM-ZF	8-DIP	-		**
HA 1202	LIN-IC	FM-ZF	8-DIP	-		**
HA 1203	LIN-IC	FM-ZF	8-DIP	-		**
HA 1211	LIN-IC	FM-ZF	8-SIP	HA 1211	8-SIP	*
HA 1306(W)	LIN-IC	NF-E, 18V, 2,25A, 3,5W(13V/4 $\Omega$ )	10-QIP+f	-		**
HA 1317(V,W,VU,WU)	LIN-IC	NF-E, 36V, 8W(26V/8 $\Omega$ )	10-DIP+g	-		**
HA 1319	LIN-IC	NF-V+E, 12V, 1W(6V/4 $\Omega$ )	14-DIP	-		**
HA 1322(W)	LIN-IC	NF-E, 18V, 2,25A, 5,5W(13V/4 $\Omega$ )	10-DIP+f	-		**
HA 1324	LIN-IC	NF-E, 18V, 2,25A, 4,5W(13V/4 $\Omega$ )	10-DIP+g	-		**
HA 1325	LIN-IC	NF-E, 20V, 1,25A, 2W(13V/8 $\Omega$ )	12-DIP+a	-		**
HA 1327	LIN-IC	4-Kanal-/channel-Decoder	16-DIP	-		**
HA 1328	LIN-IC	Matrix f. 4-Kanal-/channel-Decoder	16-DIP	-		**
HA 1329	LIN-IC	NF-E, 9V, 1,4A, 2,5W(6V/8 $\Omega$ )	12-DIP+a	-		**
HA 1333	LIN-IC	CD-4-Demodulator	16-DIP	-		**
HA 1334	LIN-IC	CD-4-Demodulator	16-DIP	-		**
HA 1338	LIN-IC	NF-E, 33V, 4,1A, 6W(24V/8 $\Omega$ )	10-QIP+f	-		**
HA 1339(A)	LIN-IC	NF-E, 18V, 4,5A, 5,5W(13V)	10-SILP+a	-		**
HA 1339(A)R	LIN-IC	=HA1339: spiegelb.Pinbel./rev.pinning	10-SILP+a	-		**
HA 1342(A)	LIN-IC	NF-E, 18V, 4,5A, 5,5W(13V)	10-SILP+a	-		**
HA 1342(A)R	LIN-IC	=HA1342: spiegelb.Pinbel./rev.pinning	10-SILP+a	-		**
HA 1345 V	LIN-IC	NF-E, 36V, 8W(26V/8 $\Omega$ )	10-SILP	-		**
HA 1350	LIN-IC	NF-E, $\pm 30V$ , 7,5A, 18W( $\pm 25V$ /8 $\Omega$ )	10-SILP	-		**
HA 1361	LIN-IC	NF-E, 9V, 2,25A, 1W(6V/4 $\Omega$ )	12-DIP+b	-		**
HA 1364	LIN-IC	TV-Ton-ZF+E, 1,5W(24V/16 $\Omega$ )	12-QIP+b	-		**
HA 1366 W	LIN-IC	NF-E, 18V, 4,5A, 5,5W(13V/4 $\Omega$ )	10-SILP+a	-		**
HA 1366 WR	LIN-IC	=HA1366W:spiegelb.Pinbel./rev.pinning	10-SILP+a	-		**
HA 1367(A)	LIN-IC	Rec., NF-V+E, 9V, 2,25A, 2,2W(6V/4 $\Omega$ )	20-DIP+b	-		**
HA 1368	LIN-IC	NF-E, 18V, 4,5A, 5,3W(13V/4 $\Omega$ )	10-SILP+a	-		**
HA 1368 R	LIN-IC	=HA1368:spiegelb.Pinbel./rev.pinning	10-SILP+a	-		**